

## ELECTRICAL CIRCUITS


2020-2021 FALL SEMESTER

### HOMEWORK #6

DUE TO: 02.02.2021 9:00 A.M.

An optional homework. +5 P will be added to the annual average of the students who submit their assignments.

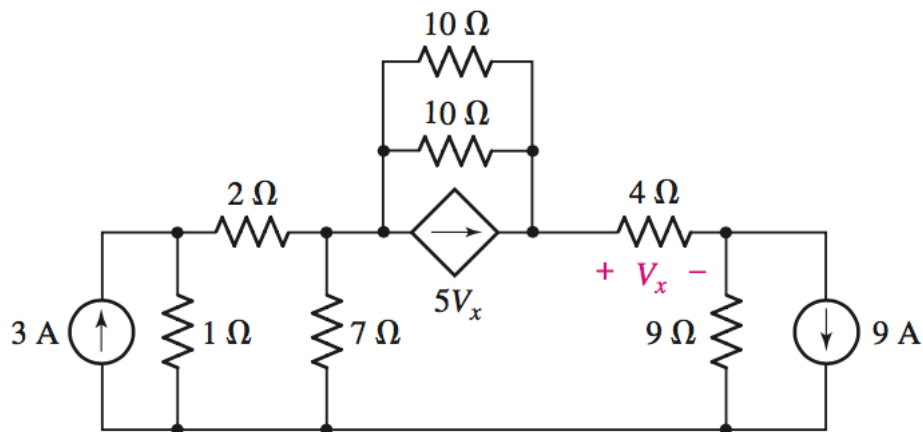1. a. Use source transformations to find  $V_x$  in the following circuit.  
b. Find the power of dependent source and determine if the source absorbs or supplies power.




2. The variable resistor  $R_0$  in the circuit below is adjusted for maximum power transfer to  $R_0$ .


a) Find the value of  $R_0$ .

b) Find the maximum power that can be delivered to  $R_0$ .

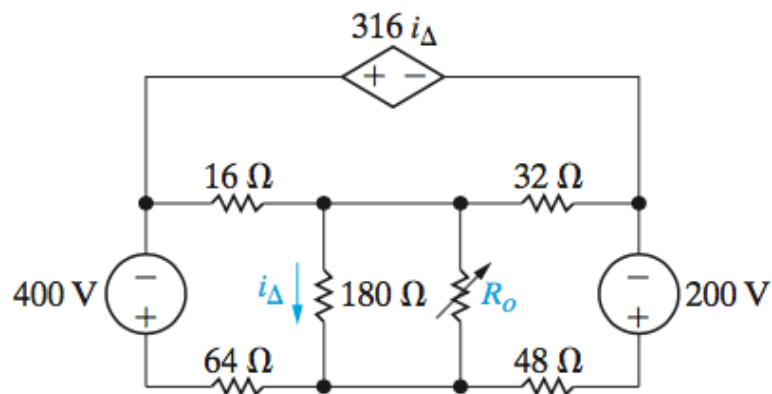c) What percentage of the total power developed in the circuit is delivered to  $R_0$  found in part(a)?



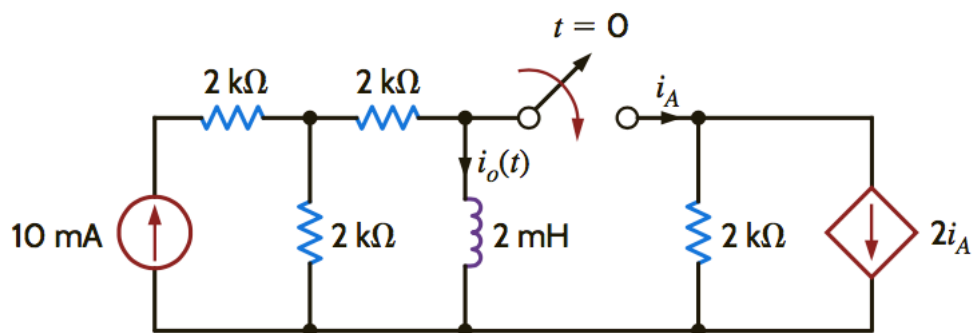3. Find  $i_o(t)$  for  $t > 0$  in the following circuit.



4. The circuit in the following has been in operation for a long time. At  $t = 0$ , the voltage source reverses polarity and the current source drops from 3 mA to 2 mA. Find  $v_o(t)$  for  $t > 0$ .

