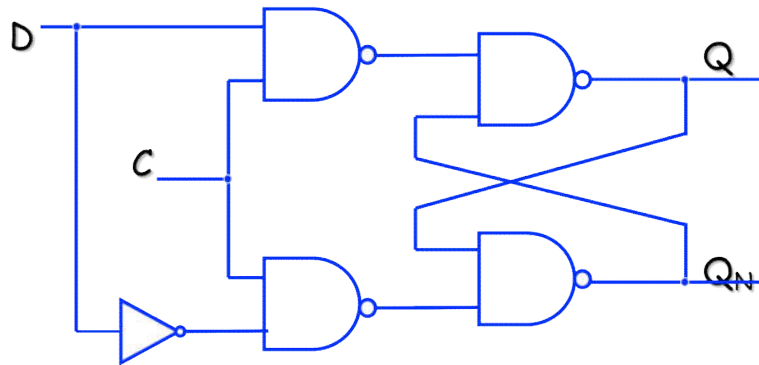


EGE UNIVERSITY
LOGIC DESIGN LABORATORY
EXPERIMENT-7

D-Latch

EXPERIMENTAL WORK

Connect the following circuit and check its operation.



Required Equipment: 7404 NOT and 7400 NAND gates. Use switches for the inputs and LEDs for the outputs.

