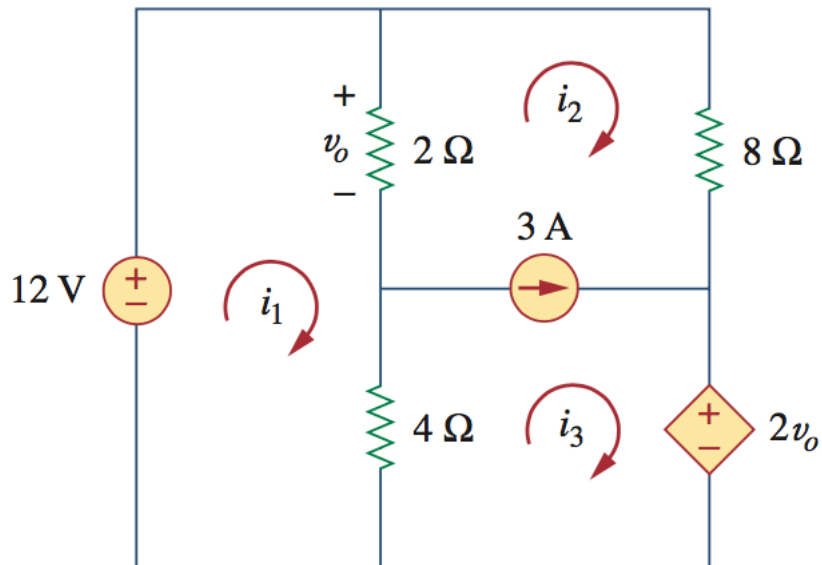


HOMEWORK 2 (ELECTRICAL CIRCUITS-2020-2021 AUTUMN SEMESTER)

Please load your hand writing solutions in pdf format to EgeDers due to date:8.12.2020 at 09:00 am.

1. Use mesh analysis to find i_1, i_2 , and i_3 in the following circuit.



2. Find v_x and i_x in the following circuit by using mesh-current method.

