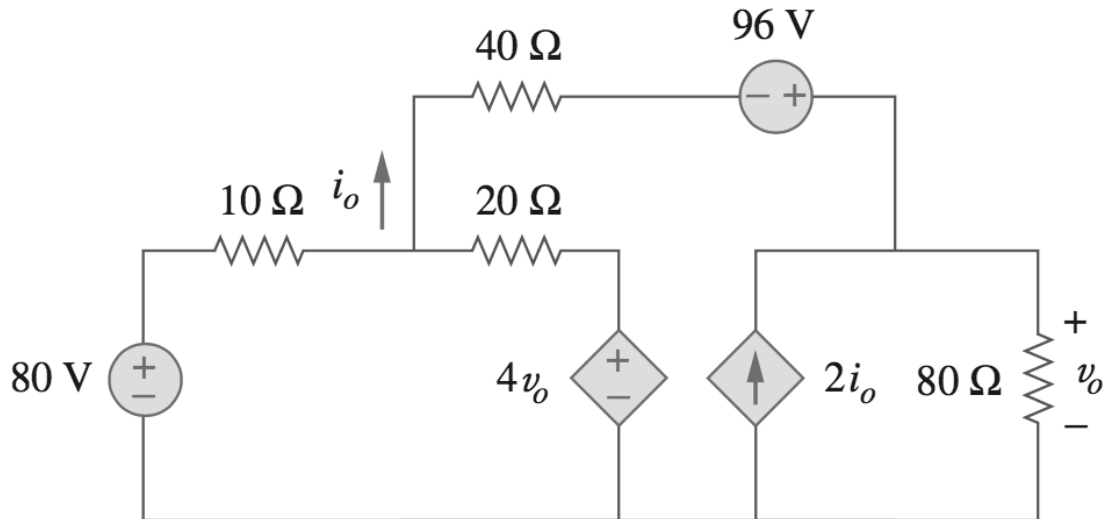


Homework 1

Please load your hand writing solutions in pdf format to EgeDers due to date:1.12.2020 at 09:00 am.

1. By using node voltage method, calculate the power of dependent current source. Determine if it absorbs or supplies energy.



2. Use the node-voltage method to find the power developed by the 20 V source in the circuit, below.

