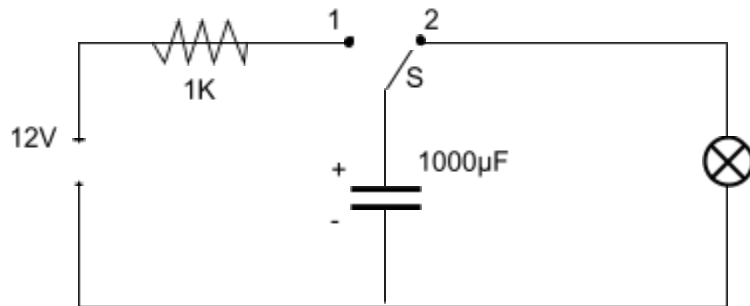


## EXPERIMENT 7

**Topic:** Observing that a capacitor can store electrical energy and transfer this energy to a load, examine current directions during capacitor charging and discharging.

Set up the circuit as shown in the figure.



1. Turn the S switch to position 1 and observe the filling of the capacitor using an avometer.
  - a) When the voltage increases on the capacitor, how much voltage is there on it? Meanwhile, what is the value of the current flowing through the capacitor?
  - b) As the voltage on the capacitor increases, does the current through it increase? Why?
2. Turn the S switch to position 2.
  - a) Did the lamp burn out? If burned, where could it get the necessary voltage?
  - b) Is the voltage on the capacitor decreasing? Meanwhile, what was the direction of the current flowing through it?
  - c) During the discharge of the capacitor, does the current decrease as the voltage on it decreases?
  - d) When the capacitor is completely discharged, what is the voltage on it and the current values passing through it?